

Module - 1

- * Current :- flow of charge.
- * Intensity of current :- Rate of flow of charge.
(strength)
 $I = Q/t$; $A = C/s$; unit :- Ampere (A).
- * The flow of 1C of charge in 1s is known as 1A.
($1A = 1C/1s$)
- * Electric potential :- Capacity of charge to do work.
 $V = W/Q$; $V = J/C$; unit :- volts (V).
- * When 1C of charge posses an energy of 1J, then the body has an electric potential of 1V.
- * Potential difference :- Force which causes the electric current flow in a closed circuit.
 $V_{ba} = V_b - V_a$.
- * Electromotive Force :- Pressure or force which causes an electric current to flow.
unit :- volt (V).
- * Power :- The rate of doing work.
 $P = VI$; $P = V^2/R$; $P = I^2R$; unit :- watts or hp or kilowatts.

1 horse power = 746 watts.
- * Energy :- Capacity to do work.
unit :- J or kWh.
 $kWh = \text{power in kW} \times \text{time in hr}$.

- Resistance :- Property of a substance to oppose the flow of electric current.
Unit: ohm (Ω).
- When 1A current flowing through a conductor produces a heat at the rate of 1J/s, then a conductor is said to have 1 Ω resistance.

Q1) Consider a resistance which is connected to a 12V supply having resistance 2 Ω , then what will be the charge produced in Coulombs for 10 sec?

Ans) $V = 12V$; $R = 2\Omega$

$$V = IR$$

$$12 = I \times 2$$

$$I = 6A$$

$$Q = ? ; t = 10s ; I = 6A$$

$$Q = It$$


$$= 10 \times 6$$

$$= \underline{\underline{60C}}$$

- Ohm's law : At a constant temperature, the ratio of potential difference (V) between any 2 points on a conductor to the current (I) flowing between them, is constant.

$$\begin{aligned} V/I &= \text{constant} \\ &= R \end{aligned}$$

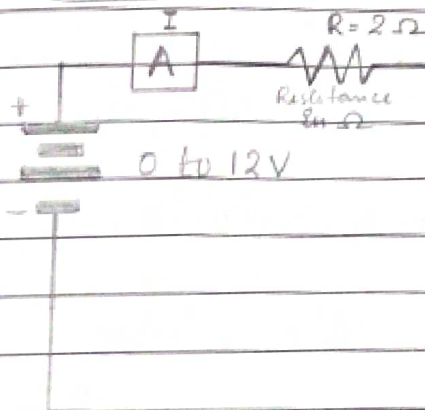
* Volt-Ampere Characteristics (VI characteristics)



V	R	$I = V/R$
0	2	0
4	2	2
10	2	5
12	2	6

$$\begin{aligned} \text{Slope} &= y/x \\ &= 1/v \\ &= 1/R \end{aligned}$$

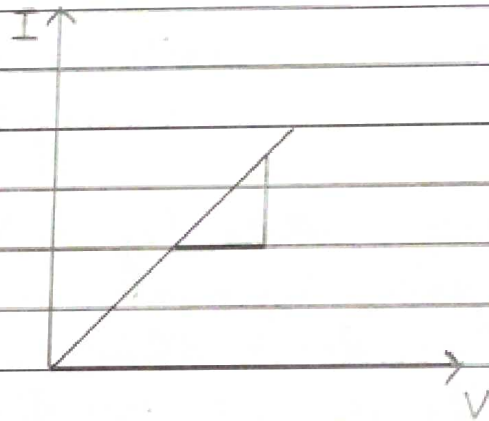- Conductance ($1/R$)
- VI characteristics of R: Shows how much current a resistor allows.



* Linear Resistance

- Resistance doesn't vary with the flow of current through it.
- The current through it, will always be proportional to the voltage applied across it.
- VI characteristic is linear
- eg: Rheostat, potentiometer

I
(current)

V
(voltage)

* Non linear Resistance

- Resistance varies with the flow of current through it.

* Non linear VI characteristics.

eg: Tungsten filament, Thermistor.

* Laws of Resistance

- The resistance offered by a conductor depends on the following factors:

- varies directly as its length, l
- varies inversely as cross sectional area, A .
- depends on the nature of material
- Also depends on the temperature θ of the conductor.

• For const temp

$$R \propto \frac{l}{A}$$

$$R = \frac{\rho l}{A}$$

- ρ is the specific resistance or resistivity.
- when $l = 1\text{m}$, $A = 1\text{m}^2$ then $R = \rho$
- ρ is the resistance between the opposite faces of 1m cube of that material.

* Conductor & Conductivity

- Reciprocal of resistance (conductance)

- Conductance is defined as the potential for a substance to conduct electricity.

$$G = \frac{1}{R}$$

$$= \frac{A}{\rho l}$$

$$= \frac{\sigma A}{l}$$

- unit of σ : $\text{ohm}^{-1}\text{m}^{-1}$ or mho/m
- unit of G : mho or S

- Inductor.

- Inductance (L): property to oppose the change in flux.
- Conductor is twisted like a coil - basic inductor
- unit: Henry (H).

- Current through an Inductor.

- According to Faraday's law

$$V = L \frac{di}{dt}$$

$$di = \frac{V}{L} dt$$

$$\int_0^t di = \frac{1}{L} \int_0^t v dt$$

$$i(t) - i(0) = \frac{1}{L} \int_0^t v dt$$

$$i(t) = \frac{1}{L} \int_0^t v dt$$

• $i(0)$ is the initial current.

• Current through the inductor dependant upon the integral of the voltage of its terminals and initial current in the coil.

* Energy Stored in an Inductor

Power,

$$P = vi$$

$$= L \frac{di}{dt} \cdot i$$

(inductor \Rightarrow instantaneous power)

$$v = L \frac{di}{dt} \quad (\text{Faraday's law})$$

Energy,

$$W = \int_0^t P \cdot dt$$

$$= \int_0^t L \frac{di}{dt} \cdot i \cdot dt$$

$$= L \int_0^t i \, di$$

changing limits,

$$\text{At } t=0 ; i=0$$

$$t=t ; i=I, \text{ DC current}$$

$$W = L \int_0^t i \, di$$

$$= \frac{1}{2} L [i^2]_0^t$$

$$= \frac{1}{2} R (I^2 - 0)$$

$$W = \frac{1}{2} R I^2$$

- If current through the inductor is constant, induced voltage = 0.
(Inductor acts as a short-circuit)

- Small change in zero time will give infinite voltage. This is practically impossible. So impulsive change in inductor current is not possible.

- A pure inductor cannot dissipate energy. Hence it is known as non-dissipative passive element.

Q1) Show that, $P = I^2 R = V^2 / R$ using Ohm's law.

Ans) $V = IR$ — (1)

$P = VI$ — (2)

From (1) Sub (1) in (2)

$$P = (IR)I$$

$$= I^2 R \text{ — (3)}$$

multiplying & dividing the 3rd eqn by R

$$P = I^2 R \times \frac{R}{R}$$

$$= \frac{(IR)^2}{R} = \frac{V^2}{R}$$

Hence proved

Q2) Calculate the resistance of 100m length of a wire having a uniform cross-sectional area of 0.1 mm^2 . If the wire is made of manganin having a resistivity of $50 \times 10^{-8} \Omega \text{ m}$. If the wire is drawn out to three times its original length, by how many times would you expect its resistance to be increased?

Ans)

$$l_1 = 100 \text{ m}$$

$$A_1 = 0.1 \text{ mm}^2$$

$$= 1 \times 10^{-7} \text{ m}^2$$

$$\rho = 50 \times 10^{-8} \Omega \text{ m}$$

$$R_1 = \frac{\rho l_1}{A_1} \quad \text{--- (1)}$$

$$= \frac{50 \times 10^{-8} \times 100}{1 \times 10^{-7}}$$

$$= 50 \times 10^{-8} \times 10^9$$

$$= \underline{\underline{500 \Omega}}$$

$$R_2 = \frac{\rho l_2}{A_2} \quad \text{--- (2)}$$

\therefore as the length is increased by 3 times, area decreases by 3 times.

$$l_2 = 3l_1 \quad \text{--- (3)}$$

$$A_2 = \frac{A_1}{3} \quad \text{--- (4)}$$

\therefore Sub (3) & (4) in (2)

$$R_2 = \frac{\rho \times 3l_1 \times 3}{A_1} = 9 \frac{\rho l_1}{A_1}$$

According to eqn ①

$$\underline{\underline{R_2 = 9R_1}}$$

* Capacitor (C)

- Capacitor consist of 2 conducting surfaces separated by a layer of insulating medium called dielectric.
- Capacitor stores electrical energy in dielectric.

* Capacitance

- Ability to store electricity
- unit - Farad, F

$$C = \frac{Q}{V}$$

- One farad is amount of capacitance when 1C charge stored with 1V across the plate.

* Voltage Across Capacitor

$$C = \frac{Q}{V} \quad \text{or} \quad C = \frac{q}{v}$$

$$i = C \frac{dv}{dt} \quad \left\{ i = \frac{dq}{dt} \right\}$$

$$dv = \frac{1}{C} i dt$$

$$\int_0^t dv = \frac{1}{C} \int_0^t i dt$$

$$v(t) - v(0) = \frac{1}{C} \int_0^t i dt.$$

$v(0)$ is consid-
ered 0

$$v(t) = \frac{1}{C} \int_0^t i dt + v(0)$$

* Energy stored in capacitor

$$P = VI = v i$$

$$= vC \frac{dv}{dt}$$

$$\left\{ i = \frac{dq}{dt} \right\}$$

Energy,

$$W = \int p dt$$

$$= \int_0^t vC \frac{dv}{dt} \times dt$$

$$= C \int_0^t v dv = C \left[\frac{v^2}{2} \right]_0^t$$

$$W = \frac{1}{2} CV^2$$

- Current in the capacitor is zero when voltage is constant.
- In a fixed capacitor, voltage cannot change abruptly.
- Capacitor can store finite amount of energy even if the current through it is zero.
- Pure capacitor never dissipate energy - non-

dissipative passive element.

Active and passive sign convention

- Active sign convention is used for the devices which deliver energy to the circuit
eg: battery
- Passive sign convention is commonly used for resistors.

Active





Passive





* Energy Sources



- Ideal voltage and Ideal current source

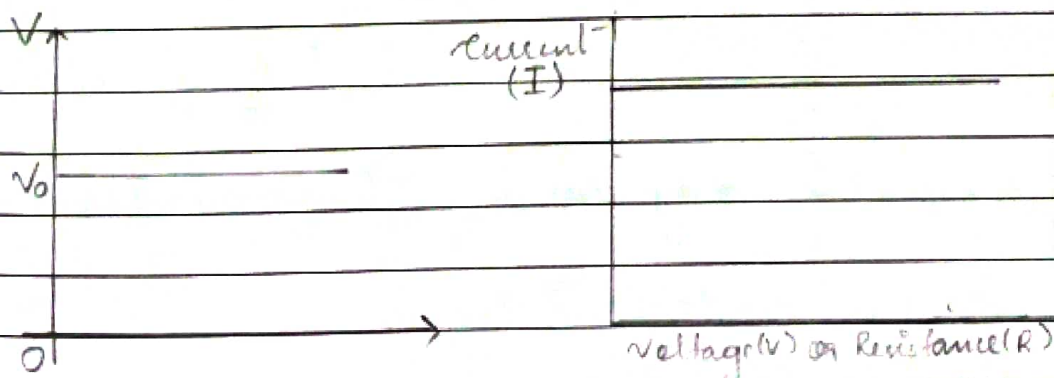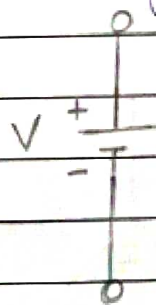

* Practical Energy sources

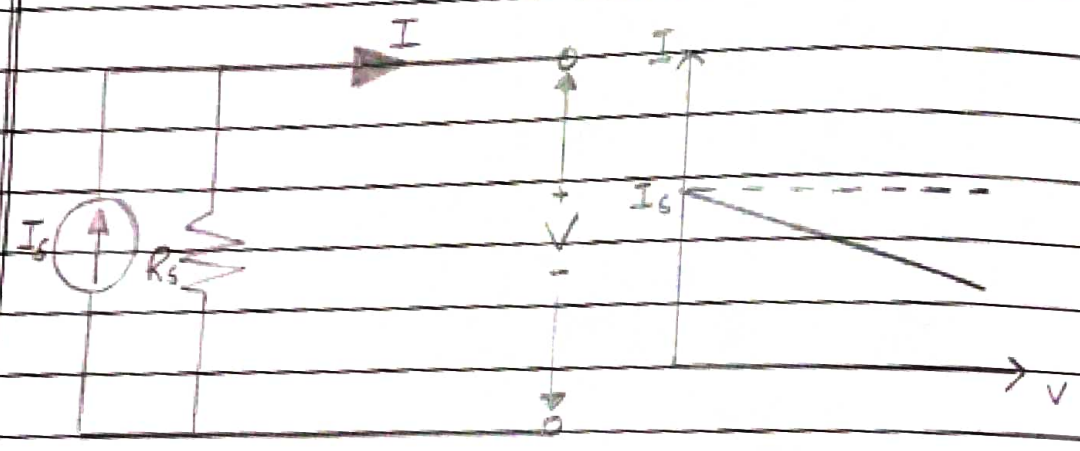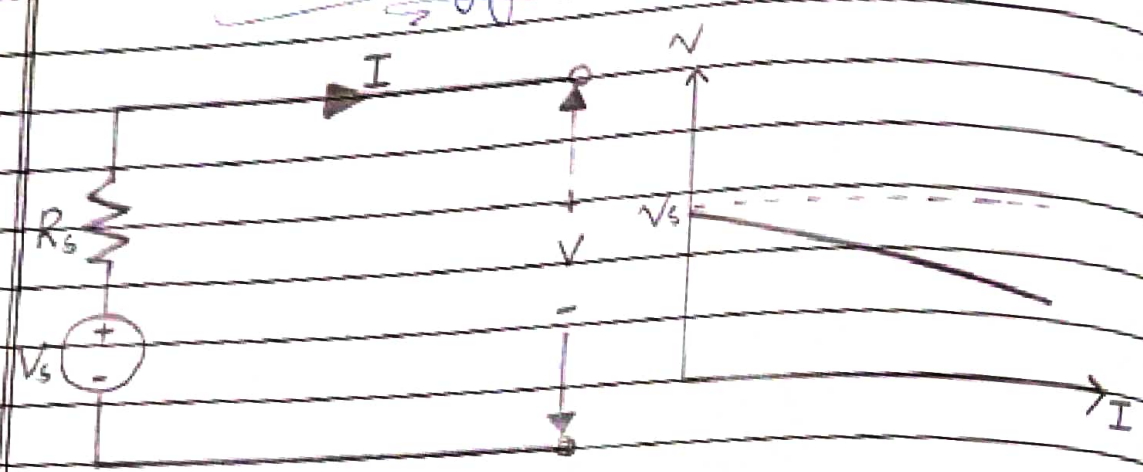

* Dependant Sources

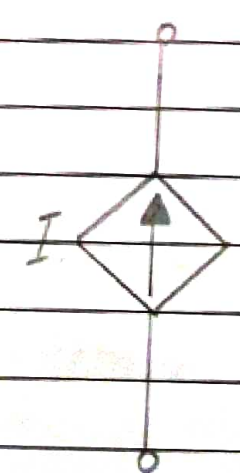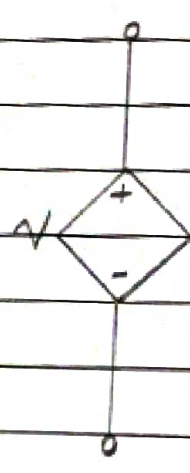

- (a) Dependent voltage source (b) Dependent current source

- Voltage controlled by voltage source.
- Voltage controlled by current source.


- Current controlled by voltage source.
- Current controlled by current source.

* Series Circuit

$$V = IR_s$$

$$\text{But } V = V_1 + V_2 + V_3$$

$$\therefore IR_s = IR_1 + IR_2 + IR_3$$

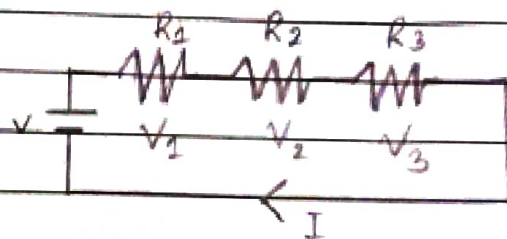

$$\text{e.g. } IR_s = I(R_1 + R_2 + R_3)$$

$$R_s = R_1 + R_2 + R_3$$

* Voltage Divider Rule

$$R = R_1 + R_2 \quad \text{--- (1)}$$


$$I = \frac{V}{R} \quad \text{--- (2)}$$

$$V_1 = IR_1$$

$$V_1 = \frac{V}{R} R_1 \quad \text{from (2)}$$

$$V_1 = \frac{R_1 V}{R}$$
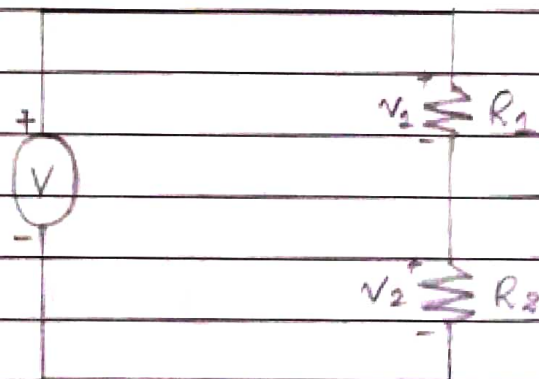
$$= \frac{R_1 V}{R_1 + R_2} \quad \text{from (1)}$$



* Parallel Circuit

$$\text{Total current} = I_1 + I_2 + I_3$$

$$I = \frac{V}{R}$$


$$\frac{V}{R_p} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

$$\left\{ V_1 = V_2 = V_3 = V \right\}$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$G = \frac{1}{R}$$


$$\therefore G_p = G_1 + G_2 + G_3$$

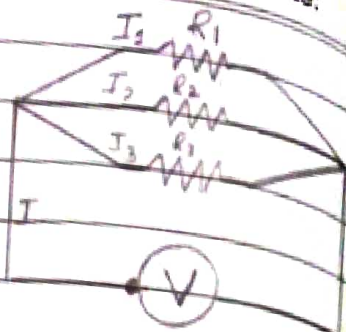

• Two Resistors in Parallel

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

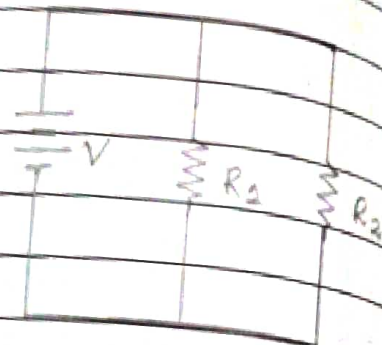


• Current division Rule

$$V = IR \quad R = \frac{R_1 R_2}{R_1 + R_2}$$

$$I_1 = \frac{V}{R_1} = \frac{IR}{R_1}$$


$$= I \times \frac{R_1 R_2}{R_1 (R_1 + R_2)}$$

$$= \frac{R_2 I}{R_1 + R_2}$$

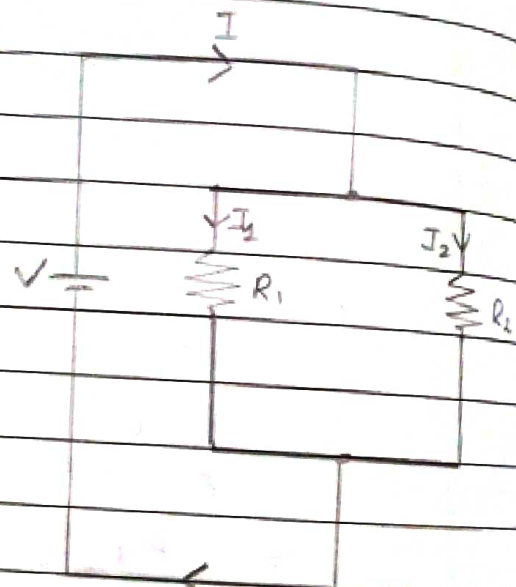

$$I_2 = \frac{V}{R_2}$$

$$= \frac{R_1 I}{R_1 + R_2}$$

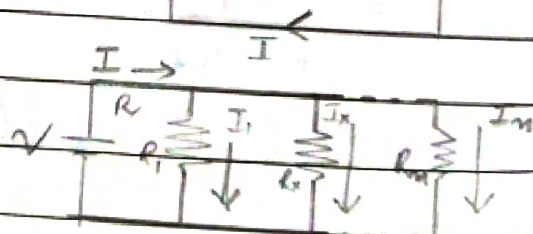

$$\therefore I_x = V/R_x$$

$$\{V = IR\}$$

$$I_x = \frac{I R}{R_x}$$

51) The resistivity of a ferric-chromium-aluminium alloy is $51 \times 10^{-8} \Omega \cdot \text{m}$. A sheet of the material is 15 cm long, 6 cm wide and 0.014 cm thick. Determine resistance between

a) opposite ends and b) opposite sides.

Ans) a) $l = 15 \text{ cm}$

$$\frac{15}{100} = 0.15 \text{ m}$$

$$A = \frac{6}{100} \times \frac{0.014}{100} = 6 \times 14 \times 10^{-7} \text{ m}^2$$


$$R = \frac{\rho l}{A}$$

$$= 51 \times 10^{-8} \times 0.15$$

$$= 51 \times 10^{-8} = \frac{6 \times 0.014}{100 \times 100} = \frac{15 \times 10000}{6 \times 100 \times 0.014}$$

$$= \frac{51 \times 15 \times 10^{-8} \times 10^3 \times 10^2}{26 \times 14}$$
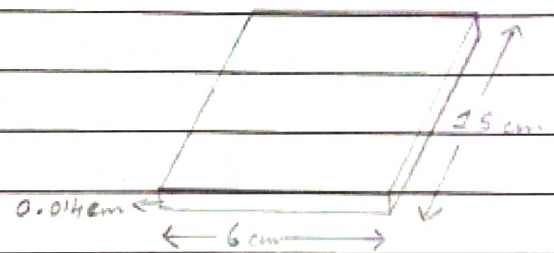
$$= \underline{\underline{9.1 \times 10^{-3} \Omega}}$$



b) $l =$

$$A = \frac{15 \times 6}{10000}$$

$$= 15 \times 6 \times 10^{-4} \text{ m}^2$$


$$R = \frac{\rho l}{A}$$

$$= 51 \times 10^{-8} \times \frac{0.014}{15 \times 6 \times 10^{-4}}$$

$$= 51 \times 10^{-8} \times \frac{14 \times 10^4}{15 \times 6 \times 1000}$$

$$= \frac{51 \times 14 \times 10^{-8} \times 10^4}{15 \times 6 \times 1000} = 7.9 \times 10^{-9} \Omega = \underline{\underline{79.3 \times 10^{-10} \Omega}}$$

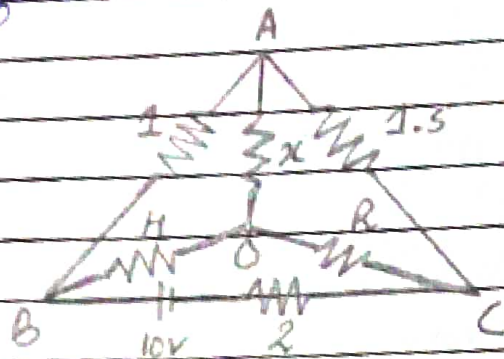Q2) Determine the value of R and current through it, if current through branch AO is zero.



Ans)

$$R_1 = 1 \Omega$$


$$R_2 = 1.5 \Omega$$

$$R_3 = 4 \Omega$$

$$R_H = R_{AO} = ?$$

$$V = 10V$$

$$R = 2 \Omega$$

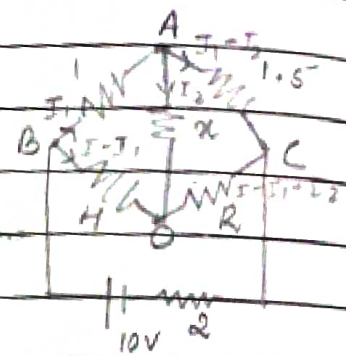

$$I_3 = 0$$

$$I - I_1 = 5 - I_1$$

$$R_1 = R_3$$

$$R_2 = R_4$$

$$\frac{1}{1.5} = \frac{4}{R_H}$$

$$R_H = 4 \times 1.5$$

$$= 6 \Omega$$

$$R_{BC} = ?$$

$$\frac{1}{R_{BC}} = \frac{1}{2.5} + \frac{1}{10}$$

$$= \frac{10 + 2.5}{25}$$

$$R_{BC} = \frac{25}{12.5} = \frac{250}{125} = 2 \Omega$$


$$\text{total resistance} = 2 + 2 = 4 \Omega$$

$$\text{total current} = \frac{V}{R_{\text{total}}}$$

$$= \frac{10}{4} = 2.5 \text{ A}$$

$$I_R = \frac{2.5 \times 2.5}{12.5} = 0.5 \text{ A}$$

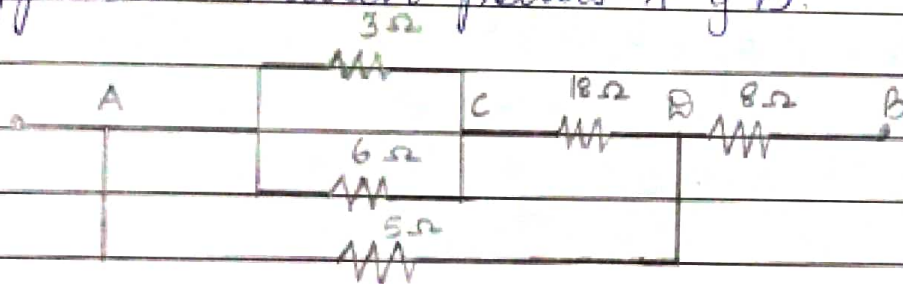93) Calculate the effective resistance of the following combination of resistances and the voltage drop across each resistance when a p.d of 60V is applied between points A & B.



Ans)


$$R_1 = 3 \Omega$$

$$R_2 = 6 \Omega$$

$$R_3 = 18 \Omega$$

$$R_4 = 5 \Omega$$

$$R_5 = 8 \Omega$$

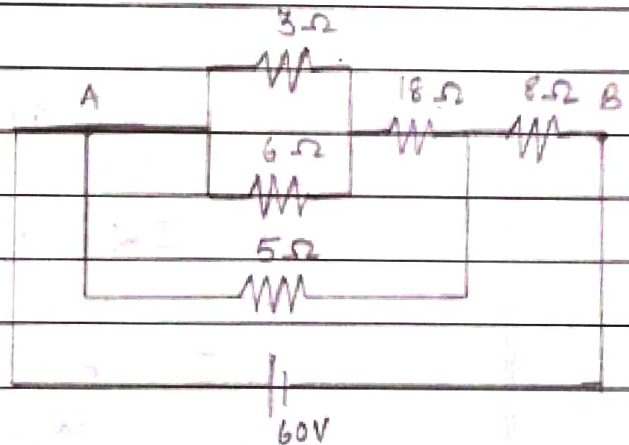

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{3} + \frac{1}{6}$$

$$= \frac{2+1}{6} = \frac{3}{6} = \frac{1}{2}$$

$$R_p = 2 \Omega$$

$$R_s = R_p + R_B$$

$$= 2 + 18 = 20 \Omega$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{20} + \frac{1}{5}$$

$$= \frac{1}{20} + \frac{4}{20}$$

$$= \frac{5}{20}$$

$$R_p = 4 \Omega$$

$$R_s = R_p + R_3$$

$$= 4 + 8$$

$$= \underline{\underline{12 \Omega}}$$

total effective resistance = 12 Ω

voltage across AB is 60V

$$V = IR$$

$$60V = I \times 12$$

$$I = \frac{60}{12} = \underline{\underline{5A}}$$

current across 5Ω resistor

$$I_x = I \times \frac{R_2}{(R_1 + R_2)}$$

$$= \frac{5 \times 20}{25}$$

$$= \underline{\underline{4A}}$$

current across 20Ω resistor
(R_1, R_2 & R_3)

$$I_y = \frac{5 \times 5}{85} \quad \left\{ \begin{array}{l} I_x = I \times R \\ R_x \end{array} \right\}$$

$$\underline{\underline{1A}}$$

\therefore voltage across ~~3~~ 3 Ω & 6 Ω resistors

$$V = IR$$

$$V = 1A \times 2\Omega$$

$$= 2V$$

$$(R_p = 2\Omega)$$

\therefore voltage across 5 Ω resistor

$$V = IR$$

$$V = 4 \times 5$$

$$= 20V$$

\therefore voltage across 18 Ω resistor

$$V = IR$$

$$= 1 \times 18$$

$$= 18V$$

\therefore voltage across 8 Ω resistor


$$V = IR$$

$$= 5 \times 8$$

$$= 40V$$

$$\left\{ I = 4 + 1 = 5A \right\}$$

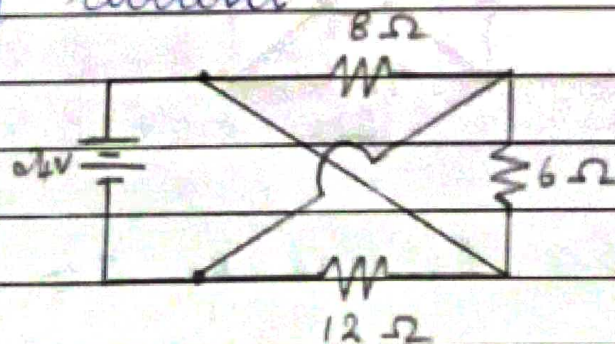
54) Compute total circuit resistance and battery current



Ans) $R_1 = 12\Omega$, $R_2 = 6\Omega$, $R_3 = 8\Omega$, $V = 24V$.

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$
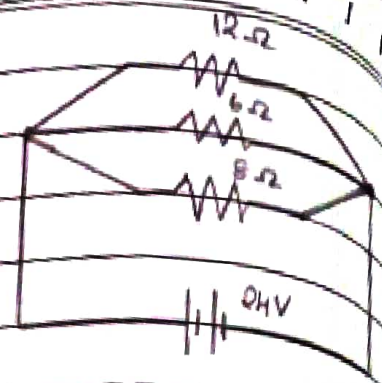
$$= \frac{1}{12} + \frac{1}{6} + \frac{1}{8}$$



$$= \frac{2+4+3}{24}$$

$$= \frac{9}{24}$$

$$R_p = \frac{24}{9} = \frac{8}{3} \Omega$$

$$V = IR$$

$$24 = I \times \frac{8}{3}$$


~~$$24 \times \frac{3}{8} = I$$~~

$$I = \frac{24 \times 3}{8}$$

~~$$I = 9A$$~~

$$I = 9A$$

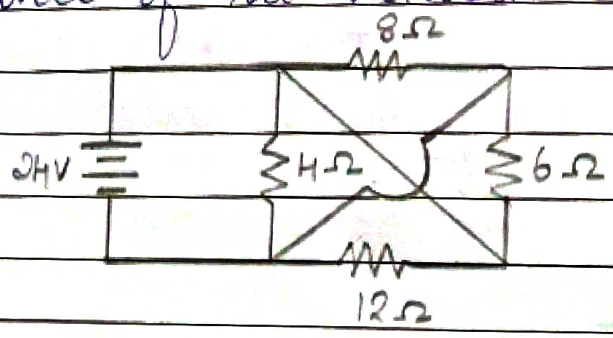Q5) Calculate battery current and equivalent resistance of the network.



Ans) $R_1 = 8\Omega$, $R_2 = 6\Omega$, $R_3 = 12\Omega$, $R_4 = 4\Omega$, $V = 24V$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

$$R_p = \frac{1}{\frac{1}{8} + \frac{1}{6} + \frac{1}{12} + \frac{1}{4}}$$

$$= \frac{24}{8+4+2+6}$$

$$= \frac{15}{24}$$


$$R_p = \frac{24^3}{15^3} \cdot \frac{8}{5} \Omega$$

$$V = IR$$


$$24 = I \times \frac{8}{5}$$

$$I = \frac{24 \times \frac{5}{8}}{1}$$

$$= \underline{\underline{15A}}$$

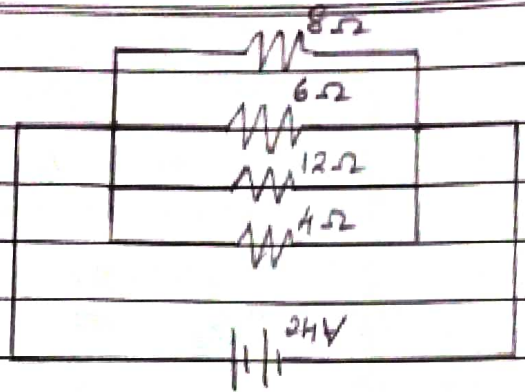

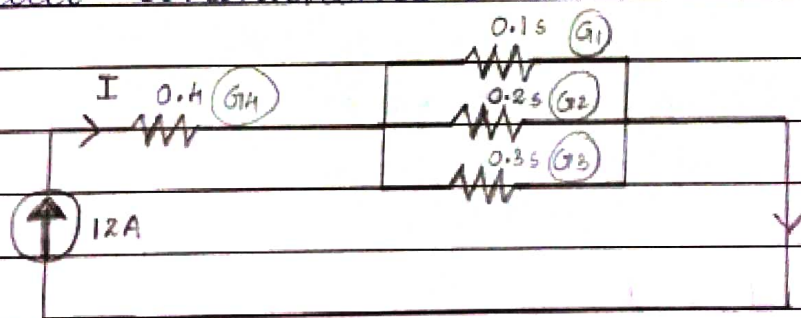9b) Calculate the values of different currents for the circuit shown in the figure, what is the total circuit conductance? and resistance?



Ans) $R = \frac{1}{G}$

$$G_p = G_1 + G_2 + G_3$$

$$= 0.1 + 0.2 + 0.3$$

$$= \underline{\underline{0.6S}}$$

$$\frac{1}{G_s} = \frac{1}{G_p} + \frac{1}{G_H}$$

$$= \frac{1}{0.6} + \frac{1}{0.4}$$

$$= \frac{4 + 6}{24}$$

$$\frac{1}{G_S} = \frac{10}{24}$$

$$G_S = \frac{24}{10} = \underline{\underline{2.4 S}}$$

$$R = \frac{10^5}{24 \times 12} = \underline{\underline{5 \Omega}}$$

$$I_x = I \times \frac{G_x}{G}$$

$$I_1 = I \times \frac{G_1}{G}$$

$$= \cancel{12} \times \frac{0.1 \times 10^5}{\cancel{24}}$$

$$= \frac{12 \times 0.1}{0.6}$$

$$= \frac{12}{6} = \underline{\underline{2 A}}$$

$$I_2 = I \times \frac{G_2}{G}$$

$$= \frac{12 \times 0.2}{0.6}$$

$$= \cancel{12}^2 \times \frac{2}{6}$$

$$= \underline{\underline{4 A}}$$


$$I_3 = I \times \frac{G_3}{G}$$

$$= \frac{12 \times 0.3}{0.6}$$

$$= \frac{12 \times 0.3}{0.6}$$

$$= \underline{\underline{6A}}$$

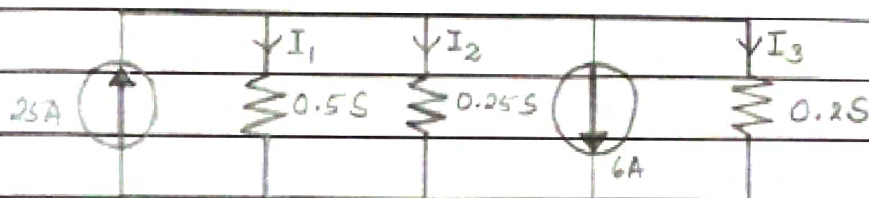Q7) Compute the values of 3 branch currents for the circuit shown. What is the P.d b/w points A & B.




Ans)

$$I = 25 - 6$$

$$= \underline{\underline{19A}}$$

$$I_1 = I \times \frac{G_1}{G}$$

- (1)

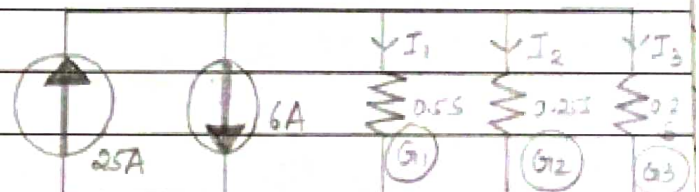

$$G = ?$$

$$G_p = G_1 + G_2 + G_3$$

$$= 0.5 + 0.25 + 0.2$$

$$= \underline{\underline{0.95S}}$$

$$\begin{array}{r} 19 \\ 5 \overline{) 95} \\ \underline{50} \\ 45 \\ \underline{45} \\ 0 \end{array}$$

$$I_1 = \frac{19 \times 0.5}{0.95}$$

$$= \frac{19 \times 50}{95}$$

$$= \underline{\underline{10A}}$$

$$I_2 = \frac{I \times G_2}{G}$$

$$= 19 \times \frac{0.25}{0.95}$$

$$= 19 \times \frac{255}{9519}$$

$$= \underline{5A}$$


$$I_a = I \times \frac{G_3}{G_1}$$

$$= 19 \times \frac{0.2}{0.95}$$

$$= 19 \times \frac{20}{9519}$$

$$= \underline{4A}$$

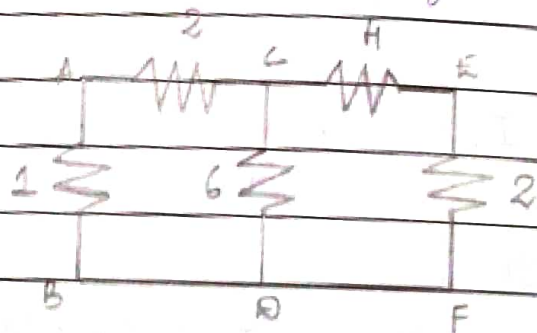Q8) Find the equivalent resistance of the circuit shown:




- (i) B/w A & B
- (ii) B/w C & D
- (iii) B/w E & F
- (iv) B/w A & F
- (v) B/w A & C.

The number represents resistances in Ω .

Ans) (i) B/w A & B.
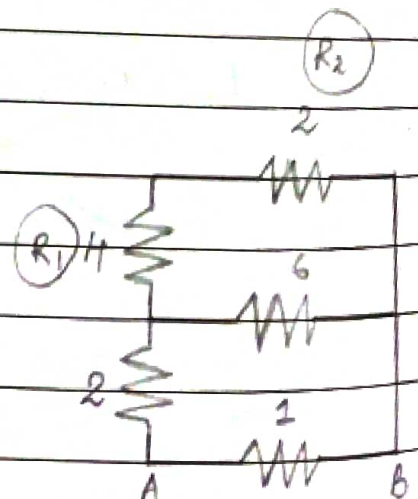
$$\begin{aligned} R_s &= R_1 + R_2 \\ &= 4 + 2 \\ &= \underline{6\Omega} \end{aligned}$$



$$\begin{aligned} 1/R_p &= 1/R_3 + 1/R_4 \\ &= 2/6 + 1/6 \\ &= 2/6 \end{aligned}$$

$$R_p = \underline{\underline{3 \Omega}}$$

$$\begin{aligned} R_s &= R_5 + R_6 \\ &= 2 + 3 \\ &= 5 \Omega \end{aligned}$$

$$\begin{aligned} 1/R_p &= 1/R_s + 1/1 \\ &= \frac{1}{5} + \frac{1}{1} \\ &= \frac{6}{5} \end{aligned}$$

$$R_p = \underline{\underline{5/6 \Omega}}$$



(ii) B/w C & D.

$$\begin{aligned} R_{s1} &= R_1 + R_2 \\ &= 4 + 2 \\ &= \underline{\underline{6 \Omega}} \end{aligned}$$

$$\begin{aligned} R_{s2} &= R_3 + R_4 \\ &= 2 + 1 \\ &= \underline{\underline{3 \Omega}} \end{aligned}$$

$$\begin{aligned} 1/R_p &= 1/R_{s1} + 1/R_5 + 1/R_{s2} \\ &= 1/6 + 1/6 + 1/3 \\ &= 2/6 + 1/3 \\ &= 4/6 \end{aligned}$$
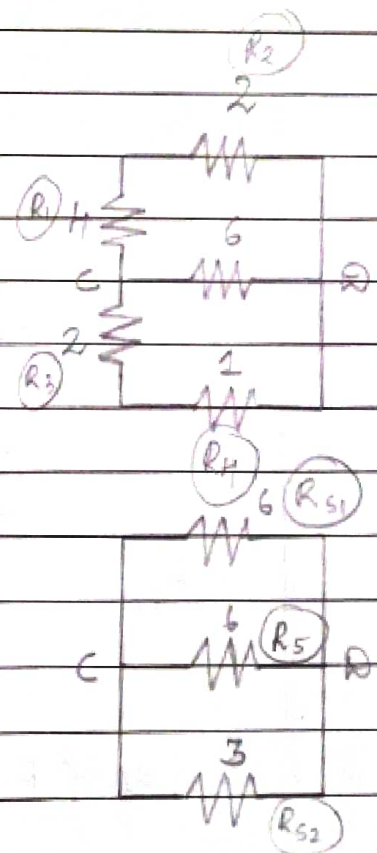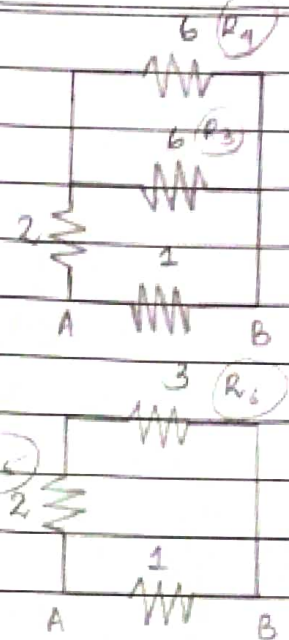
$$R_p = \frac{6}{4} = \underline{\underline{3 \Omega}}$$



(iii) B/w E & F

$$R_s = R_1 + R_2$$

$$= 2 + 1$$

$$= \underline{\underline{3 \Omega}}$$

$$\frac{1}{R_p} = \frac{1}{R_s} + \frac{1}{R_3}$$

$$= \frac{1}{3} + \frac{1}{6}$$

$$= \frac{2+1}{6}$$

$$= \frac{3}{6}$$

$$R_p = \underline{\underline{2 \Omega}}$$

$$R_{s1} = R_p + R_4$$

$$= 2 + 4$$

$$= \underline{\underline{6 \Omega}}$$




$$\frac{1}{R_{p1}} = \frac{1}{R_{s1}} + \frac{1}{R_5}$$

$$= \frac{1}{6} + \frac{1}{2}$$

$$= \frac{1}{6} + \frac{3}{2}$$

$$= \frac{4}{6}$$
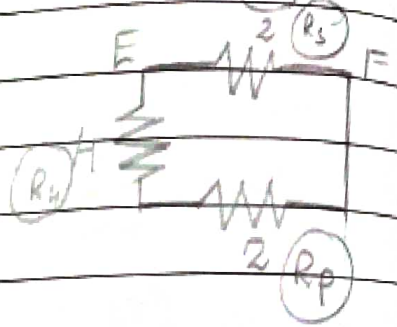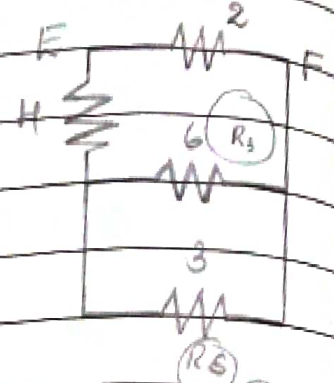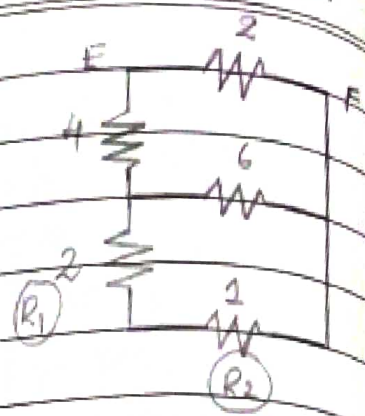
$$R_{p1} = \frac{6}{4} \Omega = \underline{\underline{\frac{3}{2} \Omega}}$$




(iv) B/w A & F

$$R_s = R_1 + R_2$$

$$= 4 + 2$$

$$= \underline{\underline{6 \Omega}}$$

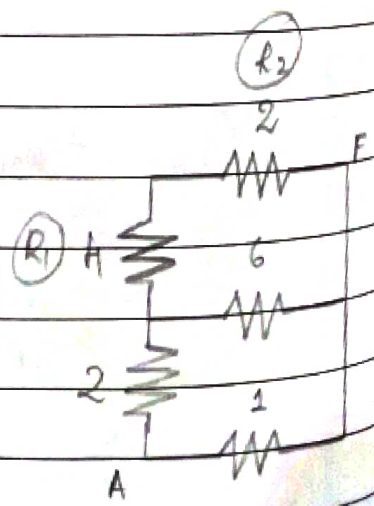


$$\begin{aligned} \frac{1}{R_p} &= \frac{1}{R_2} + \frac{1}{R_3} \\ &= \frac{1}{6} + \frac{1}{6} \\ &= \frac{2}{6} = \frac{1}{3} \end{aligned}$$

$$R_p = \underline{\underline{3\Omega}}$$

$$\begin{aligned} R_{s1} &= R_p + R_4 \\ &= 3 + 2 \\ &= \underline{\underline{5\Omega}} \end{aligned}$$

$$\begin{aligned} \frac{1}{R_{e1}} &= \frac{1}{R_{s1}} + \frac{1}{R_5} \\ &= \frac{1}{5} + \frac{1}{1} \\ &= \frac{6}{5} \end{aligned}$$

$$R_{e1} = \frac{5\Omega}{6}$$

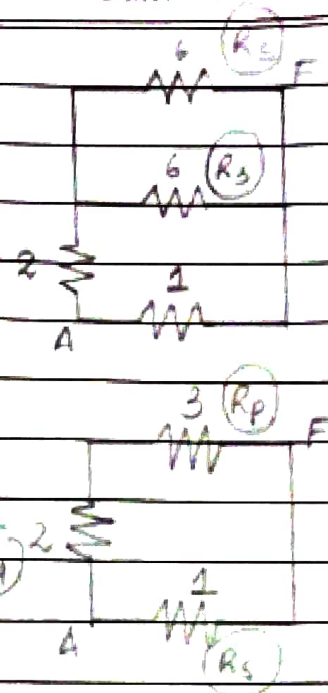


(V) B/w A & C

$$\begin{aligned} R &= R_1 + R_2 \\ &= 4 + 2 \\ &= \underline{\underline{6\Omega}} \end{aligned}$$

$$\begin{aligned} \frac{1}{R_p} &= \frac{1}{R_5} + \frac{1}{R_3} \\ &= \frac{1}{6} + \frac{1}{6} \\ &= \frac{2}{6} \end{aligned}$$

$$R_p = \underline{\underline{3\Omega}}$$
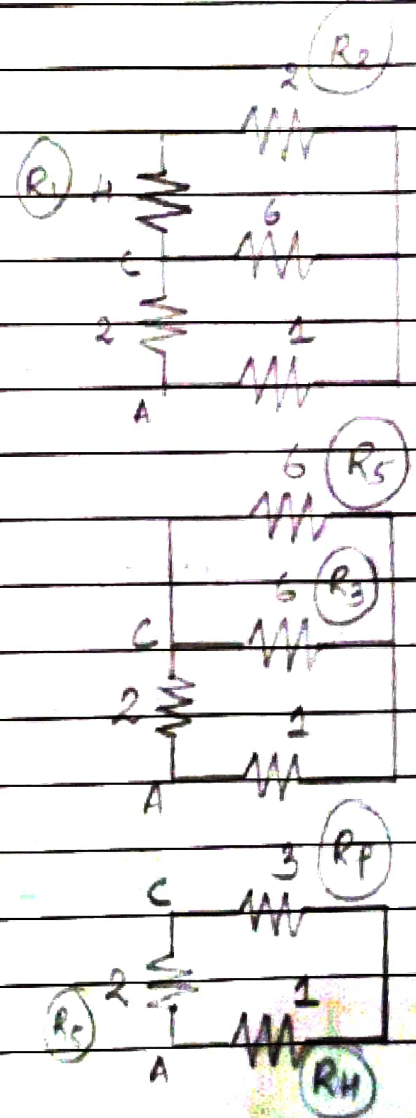
$$\begin{aligned} R_{s1} &= R_p + R_4 \\ &= 3 + 1 \\ &= \underline{\underline{4\Omega}} \end{aligned}$$




$$\frac{1}{R_p} = \frac{1}{R_4} + \frac{1}{R_5}$$

$$= \frac{1}{4} + \frac{1}{2}$$

$$= \frac{3}{4}$$

$$R_p = \frac{4}{3} \Omega$$

* Delta - Star Transformation

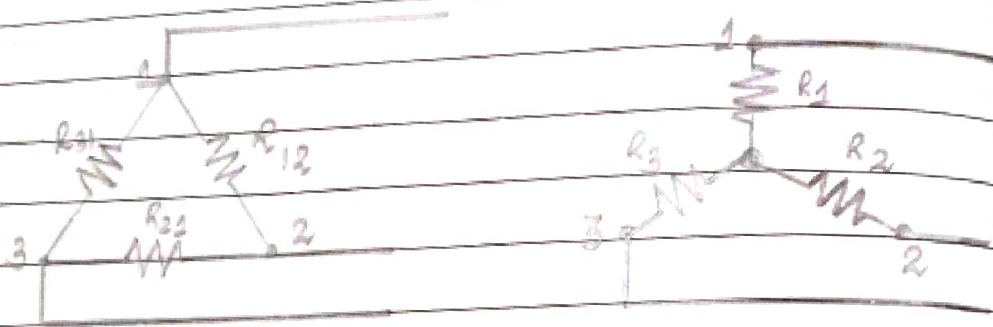


$$R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$R_2 = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{31}}$$

$$R_3 = \frac{R_{31} R_{23}}{R_{12} + R_{23} + R_{31}}$$

* Star - Delta Transformation

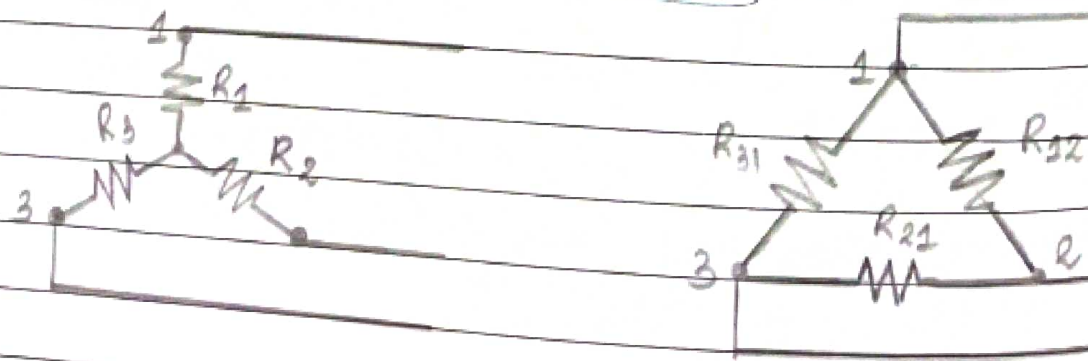

$$R_{12} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$= \frac{R_1 R_2 + R_2 + R_1}{R_3}$$

$$R_{23} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$


$$= \frac{R_2 + R_2 R_3 + R_3}{R_1}$$

$$R_{31} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$= \frac{R_1 + R_3 + R_3 R_1}{R_2}$$


Kirchhoff's Point Law or Current Law (KCL)

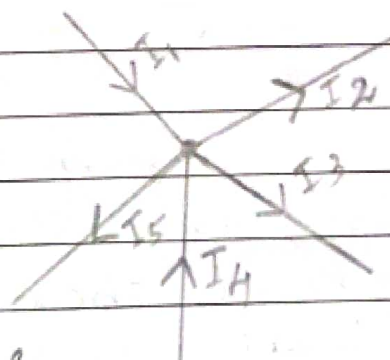- In any electrical network, the algebraic sum of the currents meeting at a point (or junction) is zero.
- Incoming currents - Outgoing currents.



$$I_1 - I_2 - I_3 + I_4 - I_5 = 0$$


$$I_1 + I_4 = I_2 + I_3 + I_5$$

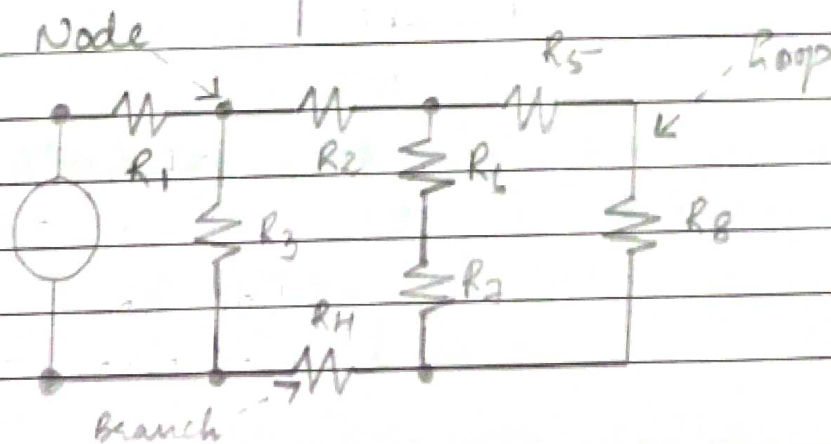

Kirchhoff's Mesh law or Voltage law (KVL)


- The algebraic sum of the products of currents and resistances in each of the conductors in any closed path (or mesh) in a network plus the algebraic sum of the e.m.f.s in that path is zero.

$$\sum IR + \sum \text{e.m.f} = 0$$

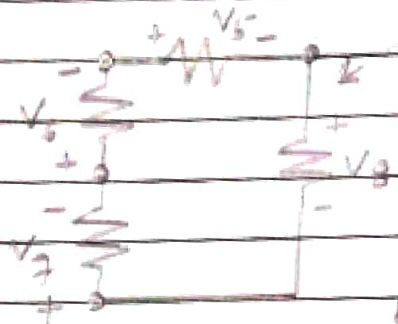

$$V_5 + V_6 + V_7 + V_8 = 0$$

Q1)

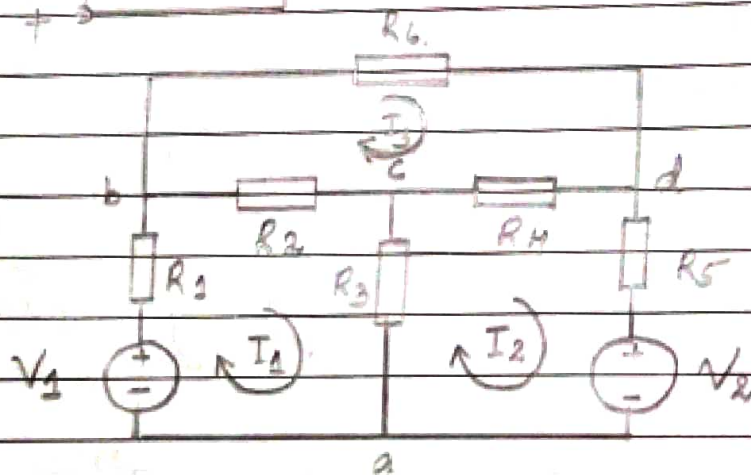

Ans)

consider loop/mesh abca.

$$-I_1 R_1 - (I_1 - I_2) R_2 - (I_1 - I_2) R_3 + V_1 = 0$$

$$-I_1 R_1 - I_1 R_2 + I_2 R_2 - I_1 R_3 + R_3 I_2 + V_1 = 0$$

$$I_1 (R_1 + R_2 + R_3) - I_2 R_3 - I_2 R_2 = V_1$$

①

Consider a c d a.

$$-(I_2 - I_1)R_3 - (I_2 - I_3)(R_4) - I_2 R_5 - V_2 = 0$$

$$I_1 R_3 - I_2 (R_3 + R_4 + R_5) + R_4 I_3 = V_2 \quad \text{--- (2)}$$

Consider b d c b.

$$-R_2(I_3 - I_1) - R_6(I_3) - R_4(I_3 - I_2) = 0$$

$$R_2 I_1 + R_4 I_2 - I_3 (R_2 + R_4 + R_6) = 0.$$

$$\text{--- (3)}$$

$$I_1 (R_1 + R_2 + R_3) - I_2 R_3 - I_3 R_2 = V_1 \quad \text{--- (1)}$$

$$I_1 R_3 - I_2 (R_3 + R_4 + R_5) + R_4 I_3 = V_2 \quad \text{--- (2)}$$

$$I_1 R_2 + I_2 R_4 - I_3 (R_2 + R_4 + R_6) = 0 \quad \text{--- (3)}$$

Matrix form:

$(R_1 + R_2 + R_3)$	$-R_3$	$-R_2$	I_1	V_1
$-R_3$	$(R_3 + R_4 + R_5)$	$-R_4$	I_2	V_2
$-R_2$	$-R_4$	$(R_2 + R_4 + R_6)$	I_3	0

* Cramer's Rule

$$ax + by = c$$

$$dx + ey = f$$

i) Write the two equations in the matrix form as

a	b	x	$=$	c
d	e	y	$=$	f

2) The common determinant is given as

$$\Delta = \begin{vmatrix} a & b \\ d & e \end{vmatrix} \\ = ae - bd.$$

3) For finding the determinant for x, replace the coefficients of x in the original matrix by the constants so that we get determinant Δ_1 given by

$$\Delta_1 = \begin{vmatrix} c & b \\ f & e \end{vmatrix} \\ = ce - bf.$$

4) For finding the determinant for y, replace coefficients of y by the constants so that we get

$$\Delta_2 = \begin{vmatrix} a & c \\ d & f \end{vmatrix} \\ = af - cd.$$


5) Apply Cramer's rule to get the value of x and y.

$$x = \frac{\Delta_1}{\Delta} = \frac{ce - bf}{ae - bd}$$

$$y = \frac{\Delta_2}{\Delta} = \frac{af - cd}{ae - bd}$$

(Similarly for 3 variables)

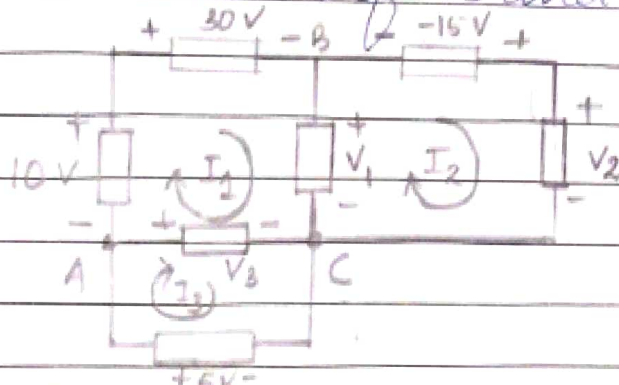Q1) Applying Kirchhoff's laws to different loops, find the values of V_1 and V_2 .



Ans) $10 - 30 - V_1 + V_3 = 0$

$$V_1 - V_3 = -20 \quad \text{--- (1)}$$

$$V_1 + 15 - V_2 = 0$$

$$V_1 - V_2 = -15 \quad \text{--- (2)}$$

$$-V_3 + 5 = 0$$

$$V_3 = 5 \quad \text{--- (3)}$$

Sub (3) in (1)

$$V_1 = -20 + V_3$$

$$= -20 + 5$$

$$= \underline{\underline{-15 \text{ V}}}$$

Sub $V_1 = -15 \text{ V}$ in (2)


$$V_1 = -15 + V_2$$

$$V_2 = +15 - 15$$

$$= \underline{\underline{0 \text{ V}}}$$

$$\therefore \underline{\underline{V_1 = -15 \text{ V} \text{ \& } V_2 = 0}}$$

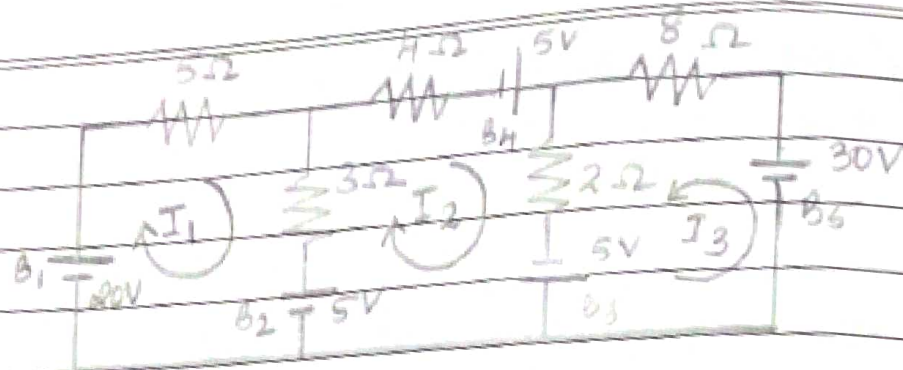Q2) Determine the current supplied by each battery in the circuit shown in the figs



Ans) Considering the 1st loop.

$$20 - 5I_1 - 3(I_1 - I_2) - 5 = 0$$

$$15 = 5I_1 + 3I_1 - 3I_2$$

$$8I_1 - 3I_2 = 15 \quad \text{--- (1)}$$

Considering the 2nd loop.

$$5 - 3(I_2 - I_1) - 4I_2 + 5 - 2(I_2 + I_3) + 5 = 0$$

$$15 - 3I_2 + 3I_1 - 4I_2 - 2I_2 - 2I_3 = 0$$

$$3I_1 - 9I_2 - 2I_3 = -15 \quad \text{--- (2)}$$

Considering the 3rd loop.

$$30 - 8I_3 - 2(I_2 + I_3) + 5 = 0$$

$$-8I_3 - 2I_2 - 2I_3 + 35 = 0$$

$$2I_2 + 10I_3 = 35 \quad \text{--- (3)}$$

$$8I_1 - 3I_2 = 15$$

$$3I_1 - 9I_2 - 2I_3 = -15$$

$$2I_2 + 10I_3 = 35$$

8	-3	0	I_1		15
3	-9	-2	I_2	=	-15
0	2	10	I_3		35

$$\begin{aligned}\Delta &= 8(-90+4) - (-3)(30) \\ &= 8 \times -86 + 90 \\ &= -688 + 90 \\ &= \underline{\underline{-598}}\end{aligned}$$

For finding I_1

$$\Delta_1 = ?$$

15	-3	0	I_1
-15	-9	-2	I_2
35	2	10	I_3

$$\begin{aligned}\Delta_1 &= 15(-90+4) - (-3)(-150+70) \\ &= -1290 - 240 \\ &= \underline{\underline{-1530}}\end{aligned}$$

$$\begin{aligned}I_1 &= \frac{\Delta_1}{\Delta} = \frac{-1530}{-598} \\ &= \frac{1530}{598} \\ &= \underline{\underline{2.55 \text{ A}}}\end{aligned}$$

For finding I_2

8	15	0
3	-25	-2
0	35	10

$$\begin{aligned}\Delta_2 &= 8(-250 + 70) - 15(30) \\ &= -640 - 450 \\ &= \underline{\underline{-1090}}\end{aligned}$$

$$\begin{aligned}I_2 &= \frac{\Delta_2}{\Delta} \\ &= \frac{-1090}{-598} \\ &= \underline{\underline{1.82A}}\end{aligned}$$

for finding I_3

8	-3	15
3	-9	-15
0	2	35

$$\begin{aligned}\Delta_3 &= 8(-9(35) + 30) - (-3)((35)3) + 15(6) \\ &= -2280 + 315 + 90 \\ &= -2280 + 405 \\ &= \underline{\underline{-1875A}}\end{aligned}$$


$$\begin{aligned}I_3 &= \frac{\Delta_3}{\Delta} \\ &= \frac{-1875}{-598} \\ &= \underline{\underline{3.13A}}\end{aligned}$$

- Current flowing through $B_1 = I_1 = 2.55A$
- Current flowing through $B_2 = I_1 - I_2 = 0.73A$
- Current flowing through $B_3 = I_2 + I_3 = 4.95A$
- Current flowing through $B_4 = I_2 = 1.82A$

Current flowing through B_5 - $I_3 = \underline{\underline{3.13 A}}$

H.W

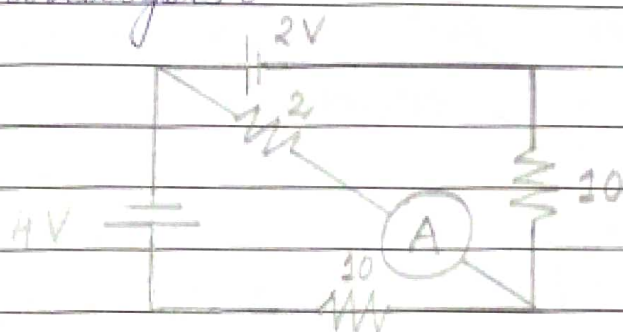Q1) Find the ammeter current in the fig using loop analysis:



Ans)

$$4 - 10I_1 - 2(I_1 - I_2) = 0$$

$$4 - 10I_1 - 2I_1 + 2I_2 = 0$$

$$-12I_1 + 2I_2 = -4$$

$$6I_1 - I_2 = +2 \quad \text{--- (1)}$$

$$2 - 2(I_2 - I_1) - 10I_2 = 0$$

$$2 - 2I_2 + 2I_1 - 10I_2 = 0$$

$$2I_1 - 12I_2 = -2$$

$$I_1 - 6I_2 = -1 \quad \text{--- (2)}$$

6	-1	I_1	=	+2
1	-6	I_2		-1

$$\Delta = -36 + 1$$

$$= -35$$

For calculating I_1

2	-1
-1	-6

$$\Delta_1 = -12 - 1$$

$$= -13$$

$$I_1 = \frac{\Delta_1}{\Delta}$$

$$= \frac{-13}{-35} = \frac{13}{35} \text{ A}$$

For calculating I_2

$$\begin{vmatrix} 6 & 2 \\ 1 & -1 \end{vmatrix}$$

$$\Delta_2 = -6 - 2$$

$$= -8$$

$$I_2 = \frac{\Delta_2}{\Delta}$$

$$= \frac{-8}{-35}$$

$$= \frac{8}{35} \text{ A}$$

\therefore the current through ammeter = $I_1 - I_2$


$$= \frac{13}{35} - \frac{8}{35}$$

$$= \frac{5}{35}$$


$$= \frac{1}{7} \text{ A}$$

2) The current is 0

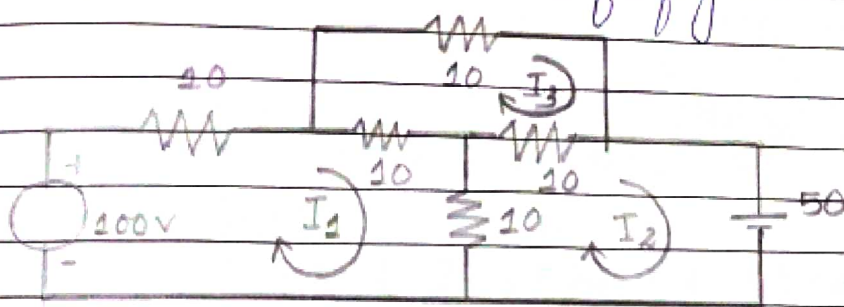53) Apply loop current method to find loop currents I_1, I_2 & I_3 in the circuit of fig 2



Ans) Considering loop 1.

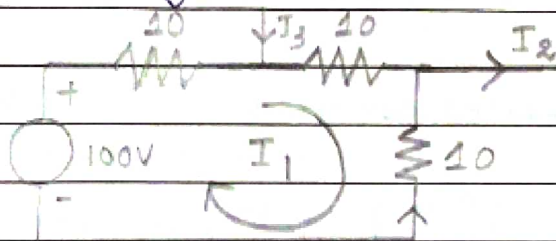


$$100 - 10(I_1) - 10(I_1 - I_3) - 10(I_1 - I_2) = 0$$

$$100 - 10I_1 - 10I_1 + 10I_3 - 10I_1 + 10I_2 = 0$$

$$30I_1 - 10I_2 - 10I_3 = 100$$

$$3I_1 - I_2 - I_3 = 10 \quad \text{--- (1)}$$

Considering loop 2

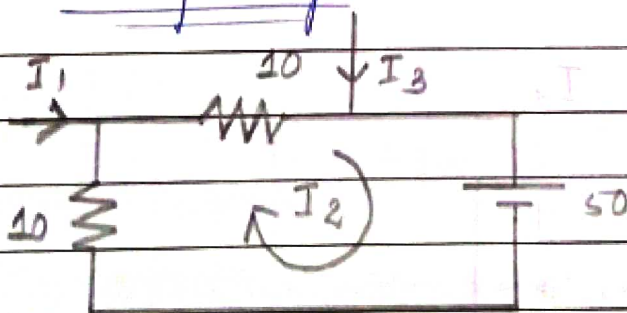


$$-50 - 10(I_2 - I_1) - 10(I_2 - I_3) = 0$$

$$-50 - 10I_2 + 10I_1 - 10I_2 + 10I_3 = 0$$

$$10I_1 - 20I_2 + 10I_3 = 50$$

$$I_1 - 2I_2 + I_3 = 5 \quad \text{--- (2)}$$

Considering loop 3

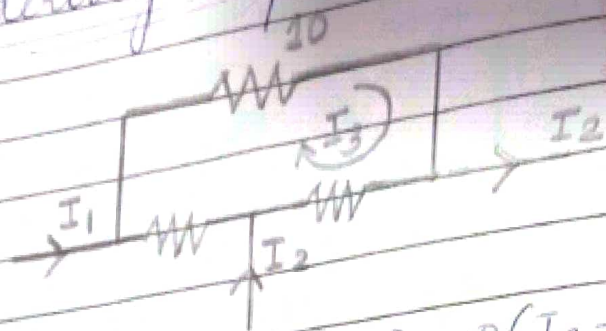

$$-10(I_3) - 10(I_3 - I_2) - 10(I_3 - I_1) = 0$$

$$-10I_3 - 10I_3 + 10I_2 - 10I_3 + 10I_1 = 0$$

$$10I_1 + 10I_2 - 30I_3 = 0$$

$$I_1 + I_2 - 3I_3 = 0 \quad \text{---(3)}$$

Matrix representation

3	-1	-1	I_1	=	10
1	-2	1	I_2	=	5
1	1	-3	I_3	=	0

$$\begin{aligned}\Delta &= 3(6-1) - (-1)(-3-1) + (-1)(1+2) \\ &= 15 - 4 - 3 \\ &= 15 - 7 \\ &= 8\end{aligned}$$

For finding I_1

10	-1	-1
5	-2	1
0	1	-3

$$\begin{aligned}\Delta_1 &= 10(+6-1) - (-1)(-15) + (-1)(5) \\ &= 50 - 15 - 5 \\ &= 50 - 20 = 30\end{aligned}$$

$$I_1 = \frac{\Delta_1}{\Delta}$$

$$= \frac{30}{8}$$

$$= \underline{\underline{3.75 A}}$$

$$\begin{array}{r} 3.75 \\ 8 \overline{) 30} \\ \underline{24} \\ 60 \\ \underline{56} \\ 40 \end{array}$$

for finding I_2

3	10	-1
1	5	1
1	0	-3

$$\Delta_2 = 3(-15) - (10)(-3) + (-1)(-5)$$

$$= -45 + 30 + 5$$

$$= \underline{\underline{0}}$$

$$I_2 = \frac{\Delta_2}{\Delta}$$

$$= \frac{0}{8} = \underline{\underline{0A}}$$

for finding I_3

3	-1	10
1	-2	5
1	1	0

$$\Delta_3 = 3(-5) - (-1)(-5) + 10(1+3)$$

$$= -15 - 5 + 40$$

$$= \underline{\underline{20}}$$

$$\begin{array}{r} 1.25 \\ 8 \overline{) 20} \\ \underline{16} \\ 4 \end{array}$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{20}{8} = \underline{\underline{1.25 A}}$$

$$\therefore I_1 = 3.25 \text{ A}$$


$$I_2 = 0 \text{ A}$$

$$I_3 = 1.25 \text{ A}$$

Mesh Analysis

- Identify the loops/meshes.
- Assign a current variable to each mesh/loop using a consistent direction (clockwise or anticlockwise).
- Write Kirchhoff's voltage law equations around each mesh.
- Solve the resulting system of equations for all mesh currents.
- Solve for other elements currents and voltages you want using Ohm's law.

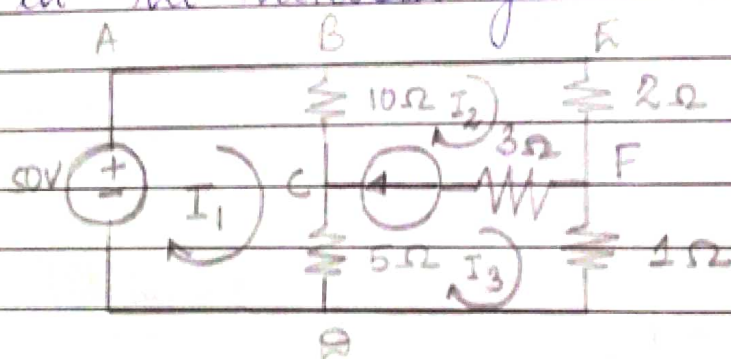Q4) Determine the current in the 5Ω resistor in the network given in fig:



Ans) Considering loop abda

$$50 - 10(I_1 + I_2) - 5(I_1 - I_3) = 0$$

$$50 - 10I_1 + 10I_2 - 5I_1 + 5I_3 = 0$$

$$10I_1 + 5I_1 - 10I_2 - 5I_3 = 50$$

$$15I_1 - 10I_2 - 5I_3 = 50$$

$$3I_1 - 2I_2 - I_3 = 10 \quad \text{--- (1)}$$

Considering loop befdcb.

$$-2(I_2) - 3(I_2 - I_3) - 10(I_2 - I_1) = 0$$

$$-2(I_2) - 1(I_3) - 5(I_3I) - 10(I_2 - I_1) = 0$$

$$-2I_2 - I_3 - 5I_3 + 5I_1 - 10I_2 + 10I_1 = 0$$

$$15I_1 - 12I_2 - 6I_3 = 0$$

$$5I_1 - 4I_2 - 2I_3 = 0 \quad \text{--- (2)}$$

$$I_2 - I_3 = 2A. \quad \text{--- (3)}$$

3	-2	-1	I_1	=	10
5	-4	-2	I_2	=	0
0	1	-1	I_3	=	2

$$\Delta = 3(4+2) - (-2)(-5) + (-1)(5)$$

$$= 18 - 10 - 5$$

$$= 18 - 15$$

$$= 3$$

3

Considering I_1 .

10	-2	-1
0	-4	-2
2	1	-1

$$\Delta_1 = 10(4+2) - (-2)(4) + (-1)(+8)$$

$$= 60 + 8 - 8$$

$$= 60$$

$$I_1 = \frac{\Delta_1}{\Delta}$$

$$= \frac{60}{3}$$

$$= \underline{20A}$$

Considering I_2

3	10	-1
5	0	-2
0	2	-1

$$\Delta_2 = 3(4) - (10)(-5) + (-1)(10)$$

$$= 12 + 50 - 10$$

$$= 12 + 40$$

$$= 52$$

$$I_2 = \frac{\Delta_2}{\Delta}$$

$$= \frac{52}{3} = \underline{17.33A}$$

Considering I_3

3	-2	10
5	-4	0
0	1	2

$$\Delta_3 = 3(-8) - (-2)(10) + 10(5)$$

$$= -24 + 20 + 50$$

$$= 70 - 24$$

$$= 46$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{46}{3} = \underline{15.33A}$$


$$\begin{aligned}
 \text{Current through } 5\Omega \text{ resistor} &= I_3 - I_2 \\
 &= 16.33 - 20 \\
 &= \underline{\underline{-4.67A}}
 \end{aligned}$$

Node Analysis

Steps to determine node voltage:

- Select a node as the reference node. Assign voltages V_1, V_2, \dots, V_{n-1} to the remaining $n-1$ nodes. The voltages are referenced with respect to the reference node.
- Apply KCL to each of the $n-1$ nonreference nodes. Use Ohm's law to express the branch current in terms of node voltages.
- Solve the resulting simultaneous equations to obtain the unknown node voltages.

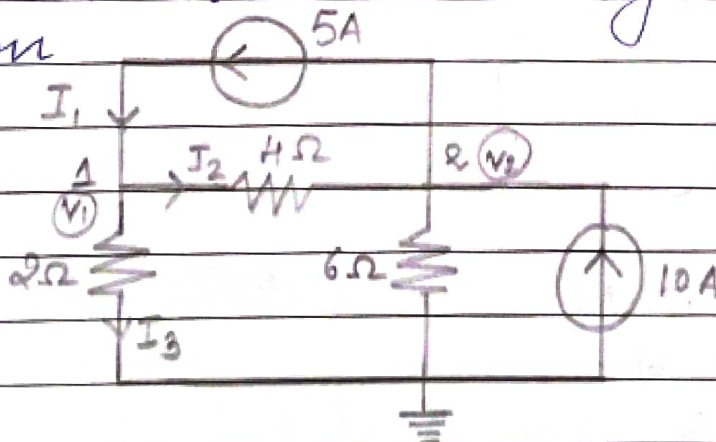Q1) Calculate the node voltages in the circuit shown



Ans) Consider node 1.

$$I_1 = I_2 + I_3$$

$$5 = \frac{V_1 - V_2}{H} + \frac{V_1}{2}$$

$$5 = \frac{V_1 - V_2 + 2V_1}{H}$$

$$20 = 3V_1 - V_2 \quad \text{--- (1)}$$

Consider node 2

$$5 - 10 + \frac{V_2 - V_1}{H} + \frac{V_2}{6} = 0$$

$$-5 + 6V_2 - 6V_1 + HV_2 = 0$$

$$10V_2 - 6V_1 = 120$$

$$5V_2 - 3V_1 = 60 \quad \text{--- (2)}$$

Using Cramer's rule

3	-1	V_1	=	20
-3	5	V_2	=	60

$$\Delta = 15 - 3 = 12$$

Finding V_1

20	-1
60	5

$$\Delta_1 = 100 + 60 = 160$$

$$V_1 = \frac{\Delta_1}{\Delta}$$

$$= \frac{160}{12} = \frac{40}{3} \text{ V}$$

Finding V_2

3	20
-3	60

180

+60

240

$$\Delta_2 = 180 + 60$$


$$= 240$$

$$V_2 = \frac{\Delta_2}{\Delta}$$

$$= \frac{240}{12} = \underline{\underline{20V}}$$

Q2) Find the branch current in the circuit of fig by using

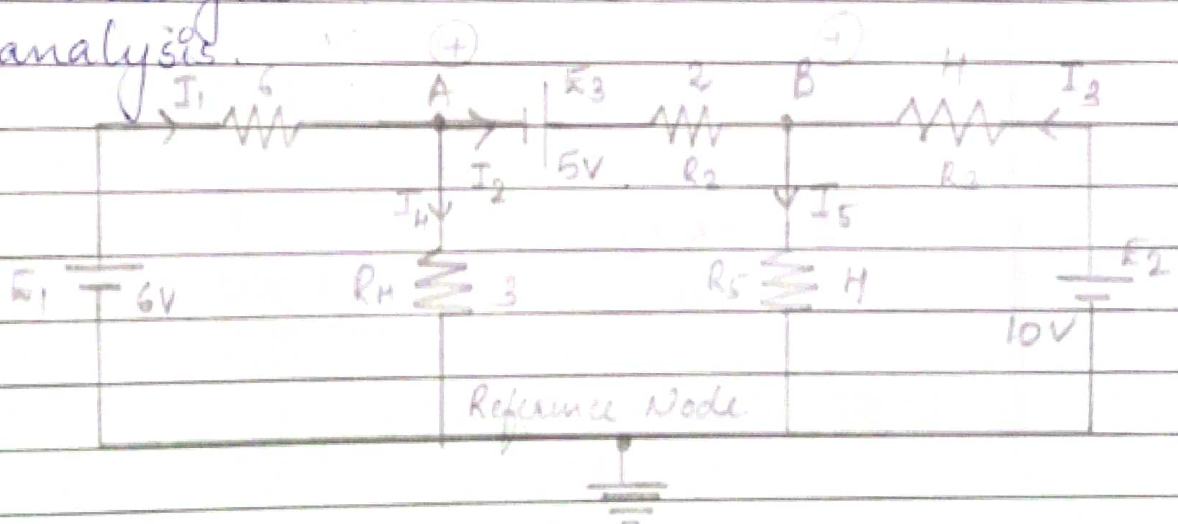- 1) Nodal analysis and
- 2) loop analysis.



Ans) 1) Consider node 1 ($V_1 > V_2$)

$$I_1 + I_2 + I_4 = 0$$

$$\frac{V_A - 6}{6} + \frac{V_A + 5 - V_B}{2} + \frac{V_A - 0}{3} = 0$$

$$V_A - 6 + 3V_A + 15 - 3V_B + 2V_A = 0$$

$$6V_A - 3V_B + 9 = 0$$

$$2V_A - V_B + 3 = 0$$

$$V_B - 2V_A = 3 \quad \text{--- (1)}$$

Considering node 2 ($V_2 > V_1$)

$$\frac{V_B - 5 - V_A}{2} + \frac{V_B}{4} + \frac{V_B - 10}{4} = 0$$

$$2V_B - 10 - 2V_A + V_B + V_B - 10 = 0$$

$$4V_B - 2V_A = 20$$

$$2V_B - V_A = 10 \quad \text{--- (2)}$$

Using Cramer's rule

-2	1	V_A	=	3
-1	2	V_B		10

$$\Delta = -4 + 1$$
$$= -3$$

Considering V_A

3	1
10	2

$$\Delta_1 = 6 - 10$$
$$= -4$$

$$V_A = \frac{\Delta_1}{\Delta} = \frac{-4}{-3} = \frac{4}{3} \text{ V}$$

Considering V_B

$$\begin{array}{|c|c|} \hline -2 & 3 \\ \hline -1 & 10 \\ \hline \end{array}$$

$$\Delta_2 = -20 + 3 \\ = -17$$

$$V_B = \frac{\Delta_2}{\Delta} \\ = \frac{-17}{-3} = \frac{17}{3} \text{ V}$$

$$I_1 = ?$$

$$I_1 = \frac{-V_A + 6}{6} \\ = \frac{-4 + 6}{6} \\ = \frac{-4 + 18}{18} \\ = \frac{+14}{18} \text{ A} = \frac{7}{9} \text{ A}$$

$$I_2 = ?$$

$$I_2 = \frac{V_A - V_B + 5}{2} \\ = \frac{4 - \frac{17}{3} + 5}{2} \\ = \frac{4 - 17 + 15}{6} = \frac{2}{6} = \frac{1}{3} \text{ A}$$

$$I_3 = ?$$

$$I_3 = \frac{-V_B + 10}{4}$$

$$= \frac{-17 + 10}{3}$$

$$= \frac{-7}{3}$$

$$= \frac{-7 + 30}{12}$$

$$= \frac{+13}{12} \text{ A}$$

$$I_H = ?$$

$$I_H = \frac{V_A}{3}$$

$$= \frac{4}{9} \text{ A}$$

$$I_5 = ?$$

$$I_5 = \frac{V_B}{4}$$

$$= \frac{17}{3 \times 4}$$

$$= \frac{17}{12} \text{ A}$$

Using loop current method:

Consider loop 1.

$$-6I_1 - 3I_H + 6 = 0 \quad -6I_1 - 3(I_1 - I_2) + 6 = 0$$

$$-6I_1 - 3I_1 + 3I_2 + 6 = 0$$

$$9I_1 - 3I_2 = 6$$

$$3I_1 - I_2 = 2 \quad \text{--- (1)}$$

Considering loop 2

$$5 + (-2I_2) - 4(I_2 - I_3) - 3(I_2 - I_1) = 0$$

$$5 - 2I_2 - 4I_2 + 4I_3 - 3I_2 + 3I_1 = 0$$

$$5 + 3I_1 - 9I_2 + 4I_3 = 0$$

$$3I_1 - 9I_2 + 4I_3 = -5 \quad \text{--- (2)}$$

Considering loop 3

$$-4I_3 - 10 - 4(I_3 - I_2) = 0$$

$$-4I_3 - 10 - 4I_3 + 4I_2 = 0$$

$$-8I_3 + 4I_2 - 10 = 0$$

~~$$-4I_3 + 8I_2 = 10$$~~

$$-8I_3 + 4I_2 = 10$$

$$-4I_3 + 2I_2 = 5 \quad \text{--- (3)}$$

From (1)

$$3I_1 - I_2 = 2$$

$$I_2 = 3I_1 - 2 \quad \text{--- (4)}$$

From (3)

$$2I_2 - 4I_3 = 5$$

$$4I_3 = 2I_2 - 5$$

$$I_3 = \frac{2I_2 - 5}{4} \quad \text{--- (5)}$$

Sub (4) & (5) in (2)

$$3I_1 - 9(3I_1 - 2) + H(2I_2 - 5) = 5$$

$$3I_1 - 27I_1 + 18 + 2I_2 \cdot 5 = 5$$

$$3I_1 - 27I_1 + 18 + 2 \cdot (3I_1 - 2) \cdot 5 = 5$$

$$3I_1 - 27I_1 + 6I_1 + 18 - 4 \cdot 5 = 5$$

$$-18I_1 + 19 = 0 \quad -18I_1 + 14 = 0$$

$$18I_1 = 19$$

$$18I_1 = 14$$

$$I_1 = \frac{19}{18} \text{ A}$$

$$I_1 = \frac{14}{18} = \frac{7}{9} \text{ A}$$

Kom (4)

$$I_2 = 3I_1 - 2 = 3 \times \frac{7}{9} - 2 = \frac{21}{9} - \frac{18}{9} = \frac{3}{9} = \frac{1}{3} \text{ A}$$

Kom (5)

$$I_3 = \frac{2I_2 - 5}{4} = \frac{2 \times \frac{1}{3} - 5}{4} = \frac{\frac{2}{3} - 5}{4} = \frac{\frac{2}{3} - \frac{15}{3}}{4} = \frac{-\frac{13}{3}}{4} = -\frac{13}{12} \text{ A}$$

$$I_H = I_1 - I_2$$

$$= \frac{7}{9} - \frac{1}{3} = \frac{7}{9} - \frac{3}{9} = \frac{4}{9} = \frac{2}{3} \text{ A}$$

$$I_G = I_2 - I_3$$


$$= \frac{1}{3} + \frac{13}{12}$$

$$= \frac{4}{12} + \frac{13}{12}$$

$$= \frac{17}{12} \text{ A}$$

Nodal Analysis or Super node method.

Q1)

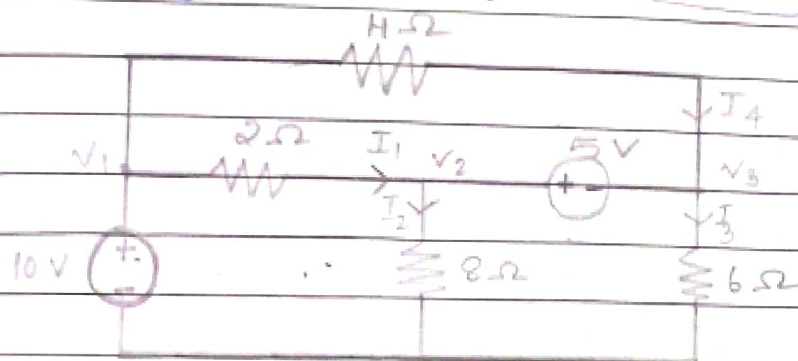

Find V_1 , V_2 & V_3 .

Ans) Considering node 1.

$$V_1 = 10V \quad - (1)$$

Considering node 2

$$\frac{V_2}{8} + \frac{(V_2 - V_1)}{2} = 0 \quad - (2)$$

Considering node 3

$$\frac{V_3}{6} + \frac{V_3 - V_1}{4} = 0 \quad - (3)$$

Adding from (2) & (3)

$$\frac{V_2}{8} + \frac{(V_2 - V_1)}{2} + \frac{V_3}{6} + \frac{(V_3 - V_1)}{4} = 0 \quad - (4)$$

$$6V_2 + 24V_2 - 24V_1 + 8V_3 + 12V_3 - 12V_1 = 0$$

$$-36V_1 + 30V_2 + 20V_3 = 0$$

$$36V_1 - 30V_2 - 20V_3 = 0$$

$$360 = 30V_2 + 20V_3$$

$$3V_2 + 2V_3 = 36 \quad \text{--- (5)}$$

considering the equation between V_2 & V_3

$$V_2 - V_3 = 5 \quad \text{--- (6)}$$

3	2	V_2	=	36
1	-1	V_3		5

$$\Delta = -3 - 2$$

$$= -5$$

Finding V_1

36	2
5	-1

$$\Delta_1 = -36 - 10$$

$$= -46$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{-46}{-5}$$

$$= \frac{46}{5}$$

Finding V_2


3	36
1	5

$$\Delta_2 = 15 - 36$$


$$= -21$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{-21}{-5} = \frac{21}{5} \text{ V}$$

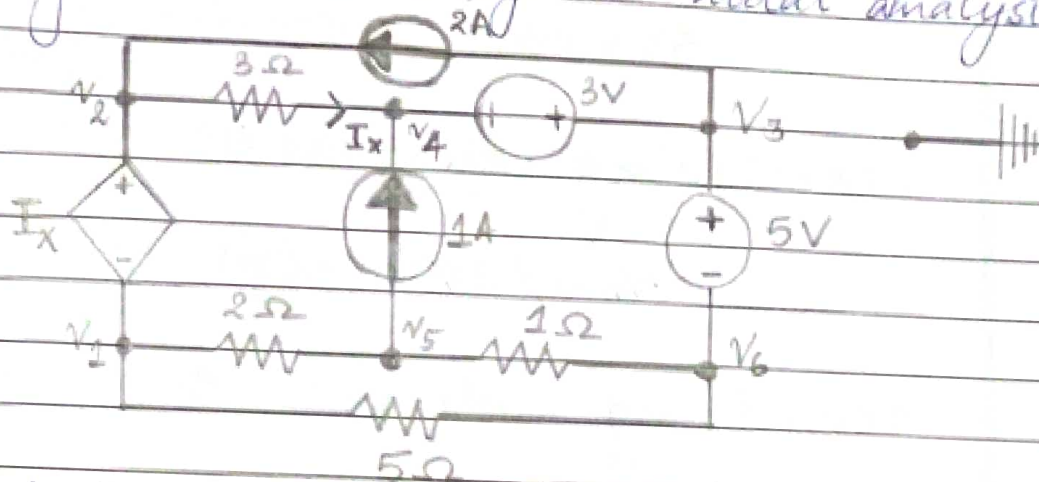5a) Determine the power of each source after solving the circuit by the nodal analysis.



Ans) Let V_3 be the reference node.

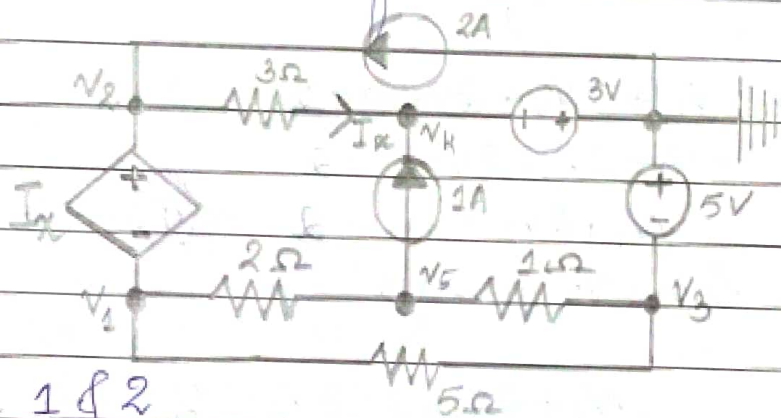

Node 1 & 2

We cannot apply KCL to this node directly due to the presence of voltage source in the branch shown.

\therefore consider 1 & 2 as supernode.

$$\frac{V_1 - V_5}{2} + \frac{V_1 - V_3}{5} + \frac{V_2 - V_4}{3} - 2 = 0$$

$$\frac{3V_1 - 3V_5 + 2V_2 - 2V_4 + V_1 - V_3 - 2 = 0}{6 \quad 5 \quad 3}$$

$$15V_1 - 15V_5 + 10V_2 - 10V_4 + 6V_1 - 6V_3 - 60 = 0$$

$$21V_1 + 10V_2 - 6V_3 - 10V_4 - 15V_5 = 60 \quad \text{--- (1)}$$

considering the node 3

$$V_3 = -5V \quad - (2)$$

considering the node 4

$$V_4 = -3V \quad - (3)$$

considering node 5

$$\frac{V_5 - V_1}{2} + \frac{V_5 - V_3}{1} + 1 = 0$$

$$V_5 - V_1 + 2V_5 - 2V_3 = -2$$

$$-V_1 - 2V_3 + 3V_5 = -2$$

$$V_1 + 2V_3 - 3V_5 = 2$$

Sub V_3 in eqn.

$$V_1 + 2(-5) - 3V_5 = 2$$

$$V_1 - 10 - 3V_5 = 2$$

$$V_1 - 3V_5 = 12 \quad - (4)$$

considering the supernode

$$I_x \Rightarrow V_2 - V_1 = 0$$

$$I_x \Rightarrow \frac{V_2 - V_4}{3} = 0$$

$$V_2 - V_1 = \frac{V_2 - V_4}{3}$$

$$3V_2 - 3V_1 = V_2 - V_4$$

$$2V_2 - 3V_1 + V_4 = 0$$

$$3V_1 - 2V_2 - V_4 = 0$$

$$3V_1 - 2V_2 = -3 \quad - (5)$$

form eqn (1)

$$21V_1 + 10V_2 + 30 + 30 - 15V_5 = 60$$

$$21V_1 + 10V_2 - 15V_5 = 0 \quad (6)$$

Sub (4) & (5) in (6)

$$21V_1 + 10(3V_1 + 3) - 15(V_1 - 12) = 0$$

$$21V_1 + 15V_1 + 15 - 5V_1 + 60 = 0$$

$$31V_1 + 75 = 0$$

$$V_1 = \frac{-75}{31}$$

$$= \underline{\underline{-2.41V}}$$

Sub $V_1 = -2.41$ in (5)

$$3(-2.41) - 2V_2 = -3$$

$$2V_2 = 3(-2.41) + 3$$

$$V_2 = (-7.23 + 3)/2$$

$$= \underline{\underline{-4.23V/2}} = \underline{\underline{-2.115V}}$$

Sub $V_1 = -2.41$ in (4)

$$V_1 - 3V_5 = 12$$

$$3V_5 = -2.41 - 12$$

$$V_5 = \frac{-2.41 - 12}{3}$$

$$= \underline{\underline{-14.41/3}} = \underline{\underline{-4.803V}}$$

Date: _____
 $V_1 = -2.41V$

$$V_2 = -2.115V$$

$$V_3 = -5V$$

$$V_4 = -3V$$

$$V_5 = -4.803V$$

$$P_{2A} = ?$$

$$V_{2A} = -V_2$$

$$= -(-2.115) = 2.115V$$

$$P_{2A} = I_{2A} V_{2A}$$

$$= 2 \times -V_2$$

$$= 2 \times 2.115$$

$$= \underline{4.230W}$$

$$P_{1A} = ?$$

$$V_{1A} = (V_5 - V_4)$$

$$= (-4.803 + 3)$$

$$= -1.803V$$

$$P_{1A} = I_{1A} \times V_{1A}$$

$$= 1 \times -1.803$$

$$= \underline{-1.803W}$$

$$P_{5V} = ?$$

$$I_{5V} = I_{1\Omega} + I_{3\Omega}$$

$$= V_3 - V_5 + \frac{V_3 - V_1}{5}$$

5

$$= \frac{5V_3 - 5V_5 + V_3 - V_1}{5}$$

$$= \frac{6V_3 - 5V_5 - V_1}{5}$$

$$= \frac{6(-5) - 5(-4.803) - (-2) \cdot 41}{5}$$

$$= \frac{-30 + 24.015 + 84}{5}$$

$$= \frac{-10.985}{5} - 3.575 \text{ A}$$

$$P_{5V} = V_{5V} \times I_{5V}$$

$$= 5 \times \frac{-3.575}{5}$$

$$= \underline{\underline{-3.575 \text{ W}}}$$

$$P_{3V} = ?$$

$$I_{3V} = I_{3\Omega} \mp 1 \text{ A}$$

$$= \frac{V_H - V_2 \mp 1}{3}$$

$$= \frac{V_H - V_2 \mp 3}{3}$$

$$= \frac{-3 + 2.115 \mp 3}{3}$$

$$= \frac{-6 + 2.115}{3} \text{ A}$$

$$P_{3V} = V_{3V} I_{3V}$$

$$= 3 \times \frac{2.115 - 6}{3}$$

$$= \underline{\underline{-3.885 \text{ W}}}$$

$$P_x = V_x I_x$$

$$\begin{aligned} V_x &= V_2 - V_1 \\ &= -2.115 + 2.41 \\ &= \underline{\underline{-0.295 \text{ V}}} \end{aligned}$$

$$\begin{aligned} I_x &= I_{2A} + I \\ &= 2 + (V_2 - V_1) \\ &= 2 + (-0.295) \\ &= 1.705 \text{ A} \end{aligned}$$

$$\begin{aligned} P_x &= V_x I_x \\ &= 0.295 \times 1.705 \\ &= \underline{\underline{0.502 \text{ W}}} \end{aligned}$$